
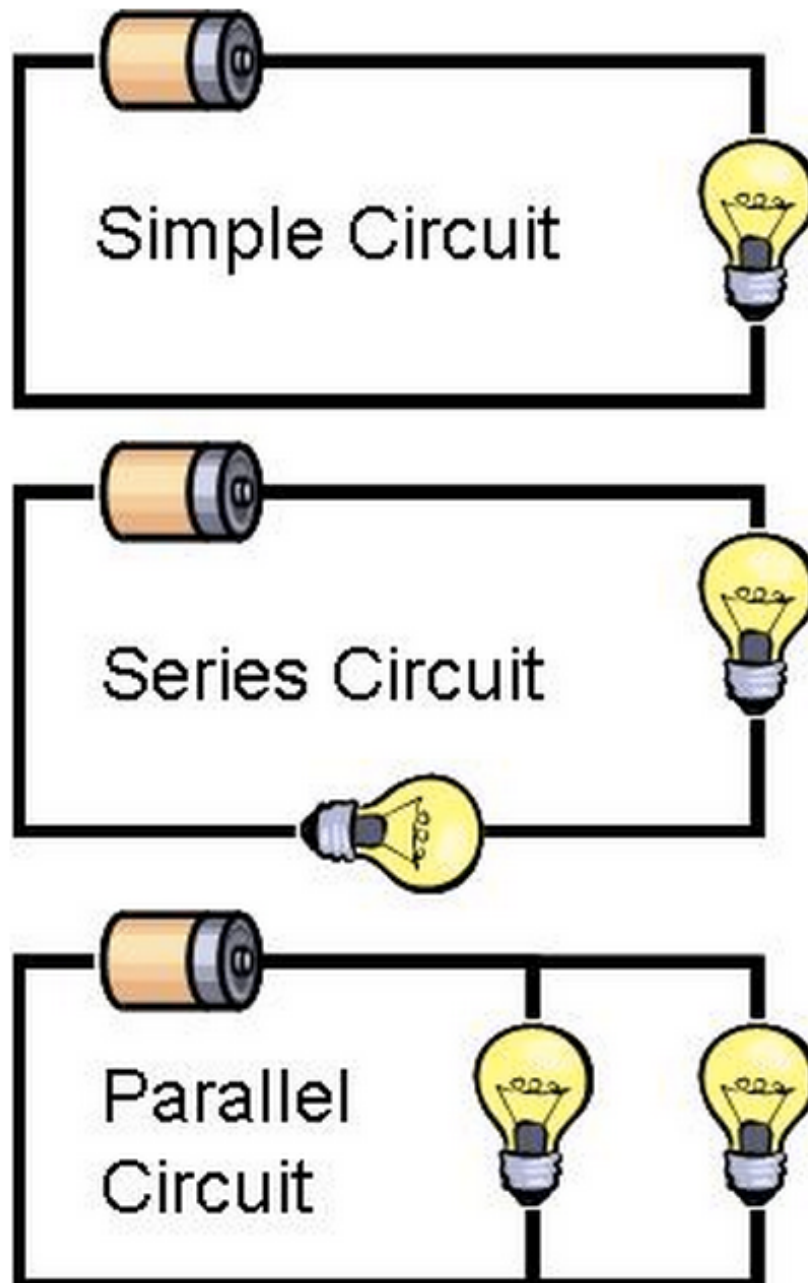


Using Circuits to Tell your Story With Fashion Tech

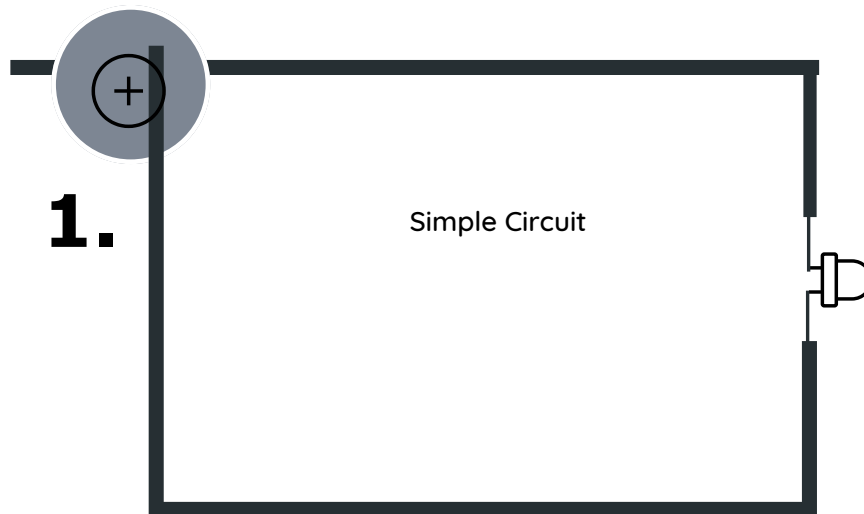
A circuit is a loop through which current can flow. A power source, such as a battery, provides the energy for the circuit to work. Electrons flow from the negative side of the power source, through the circuit and back to the positive side of the power source. Once the electrons return to the power source, the circuit is complete.



Paper Circuit Practice



Parallel Circuit

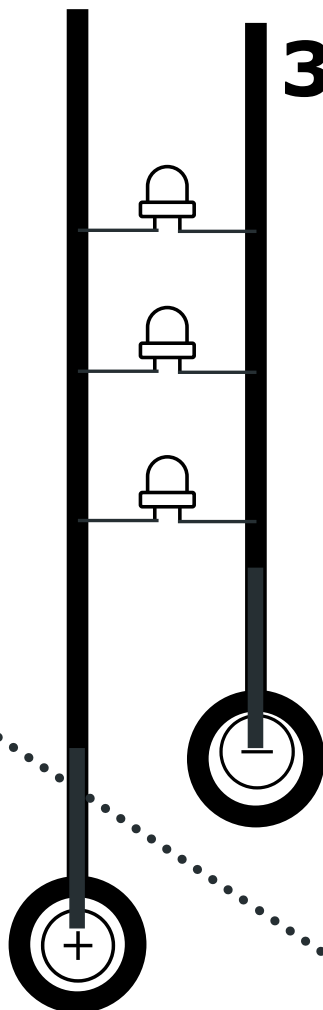

Stick the copper tape along the black lines. Use a little piece of transparent tape to put over the LED legs. Make sure the long leg is on the positive (+) side.

Put the battery with the negative side down and fold up the paper so the tape touches the positive side which is facing up.

Which kind of circuit lights up the brightest?

2.

Series Circuit

